






This document is a part of Main Course File		Document No.: CFM – 8
	<b>SARDAR VALLABHBHAI PATEL EDUCATION SOCIETY MANAGED</b>	
	<b>N. G. PATEL POLYTECHNIC</b>	
<b>ELECTRICAL ENGINEERING DEPARTMENT</b>		
<b>ASSIGNMENT</b>		
<b>Course Name (With Code):</b> Fundamentals Of Electronics (4330904)		
<b>Semester / Year:</b> Third / Second		
<b>Assignment Number:</b> 1		
<b>Assignment CO Number:</b> 4330904.1		
<b>Sr. No.</b>	<b>Questions related to Course Outcomes</b>	
<b>Part – A</b>	<b>Questions carrying 3 Marks</b>	
1	Draw and compare energy band diagram of conductor, semiconductor and insulator material.	
2	Explain full wave rectifier with two diodes giving necessary waveforms.	
3	Define Intrinsic and extrinsic semiconductor	
4	P type, N type semiconductors.	
5	Explain working of PN junction diode.	
<b>Part – B</b>	<b>Questions carrying 4 Marks</b>	
1	Explain the V-I characteristics of PN junction diode.	
2	Compare Half wave rectifier and full wave center tap rectifier.	
3	Explain forward biased PN junction diode.	
4	Explain bridge rectifier giving necessary waveforms	
5	Explain filter circuits.	
<b>Part – C</b>	<b>Questions carrying 7 Marks</b>	
1	What is rectifier circuit? Draw and Explain full wave rectifier circuit with its advantage and disadvantage.	
2	What is rectifier circuit? Compare Half wave, Full wave and Bridge Rectifier Circuit.	
3	What is the need of filter in rectifier? Enlist type of filter circuit and explain	
4		
5		
Mr. Mahendra G. Vasava		
<b>Prepared By: (Name of Faculty (ies)) with signature</b>		<b>Signature of Head of Department</b>

This document is a part of Main Course File		Document No.: CFM – 8
	<b>SARDAR VALLABHBHAI PATEL EDUCATION SOCIETY MANAGED</b>	
	<b>N. G. PATEL POLYTECHNIC</b>	
<b>ELECTRICAL ENGINEERING DEPARTMENT</b>		
<b>ASSIGNMENT</b>		
<b>Course Name (With Code):</b> Fundamentals Of Electronics (4330904)		
<b>Semester / Year:</b> Third / Second		
<b>Assignment Number:</b> 2		
<b>Assignment CO Number:</b> 4330904.2		
<b>Sr. No.</b>	<b>Questions related to Course Outcomes</b>	
<b>Part – A</b>	<b>Questions carrying 3 Marks</b>	
1	Define $\alpha$ and $\beta$ for transistor. Derive relation between $\alpha$ and $\beta$ .	
2	Compare the three configuration of transistor.	
3	Explain working of PNP transistor.	
4	Explain Class B Push Pull amplifier.	
5	Explain DC load line and define Operating point.	
<b>Part – B</b>	<b>Questions carrying 4 Marks</b>	
1	Explain working NPN transistor.	
2	What is the need of cascading in amplifiers? Draw and explain the circuit of two stages LC coupled Amplifier.	
3	Explain input and output characteristics of common base transistor configuration.	
4	With circuit & waveforms explain working of common emitter transistor amplifier.	
5	List the biasing methods of Transistor & explain any one.	
<b>Part – C</b>	<b>Questions carrying 7 Marks</b>	
1	Explain DC load line and define operating point.	
2	Draw and explain transistor as a switch.	
3	Draw the input and output characteristic of transistor in CE configuration and explain.	
4		
5		
Mr. Mahendra G. Vasava		
<b>Prepared By: (Name of Faculty (ies)) with signature</b>		<b>Signature of Head of Department</b>

<b>This document is a part of Main Course File</b>		<b>Document No.: CFM – 8</b>	
	<b>SARDAR VALLABHBHAI PATEL EDUCATION SOCIETY MANAGED</b>		
	<b>N. G. PATEL POLYTECHNIC</b>		
<b>ELECTRICAL ENGINEERING DEPARTMENT</b>			
<b>ASSIGNMENT</b>			
<b>Course Name (With Code):</b> Fundamentals Of Electronics (4330904)			
<b>Semester / Year:</b> Third / Second			
<b>Assignment Number:</b> 3			
<b>Assignment CO Number:</b> 4330904.3			
<b>Sr. No.</b>	<b>Questions related to Course Outcomes</b>		
<b>Part – A</b>	<b>Questions carrying 3 Marks</b>		
1	Define and classify different types of oscillators.		
2	Explain RC phase shift oscillator.		
3	Explain Wien Bridge oscillator.		
4	Explain the principle of Oscillator.		
5	Explain piezoelectric effect.		
<b>Part – B</b>	<b>Questions carrying 4 Marks</b>		
1	Explain Hartley oscillator with circuit diagram.		
2	Explain RC phase shift oscillator.		
3	Explain Colpitts oscillator with circuit diagram..		
4	What is Oscillator? Give classification of oscillators on different basis.		
5	State different applications of oscillators.		
<b>Part – C</b>	<b>Questions carrying 7 Marks</b>		
1	Explain crystal oscillator.		
2	Draw and explain damped oscillator in LC tank circuit.		
3			
4			
5			
<p style="text-align: center;">Mr. Mahendra G. Vasava</p>			
<b>Prepared By: (Name of Faculty (ies)) with signature</b>		<b>Signature of Head of Department</b>	

This document is a part of Main Course File		Document No.: CFM – 8
	<b>SARDAR VALLABHBHAI PATEL EDUCATION SOCIETY MANAGED</b>	
	<b>N. G. PATEL POLYTECHNIC</b>	
<b>ELECTRICAL ENGINEERING DEPARTMENT</b>		
<b>ASSIGNMENT</b>		
<b>Course Name (With Code):</b> Fundamentals Of Electronics (4330904)		
<b>Semester / Year:</b> Third / Second		
<b>Assignment Number:</b> 4		
<b>Assignment CO Number:</b> 4330904.4		
<b>Sr. No.</b>	<b>Questions related to Course Outcomes</b>	
<b>Part – A</b>	<b>Questions carrying 3 Marks</b>	
1	Explain Zener diode as a voltage regulator.	
2	Explain Photovoltaic cell.	
3	Explain working of LED.	
4	Explain working of LCD display.	
5	Write short note on UJT.	
<b>Part – B</b>	<b>Questions carrying 4 Marks</b>	
1	Explain the construction and working of N-channel JEFT.	
2	Explain AC Load control using DIAC and TRIAC.	
3	Explain P channel FET.	
4	Write the application of FET.	
5	Explain construction and working of Photo transistor.	
<b>Part – C</b>	<b>Questions carrying 7 Marks</b>	
1	Explain construction and working of SCR by using two transistor analogy with necessary diagrams.	
2	Draw and explain opto-couplers in detail.	
3		
4		
5		
Mr. Mahendra G. Vasava		
<b>Prepared By: (Name of Faculty (ies)) with signature</b>		<b>Signature of Head of Department</b>

This document is a part of Main Course File		Document No.: CFM – 8
	<b>SARDAR VALLABHBHAI PATEL EDUCATION SOCIETY MANAGED</b>	
	<b>N. G. PATEL POLYTECHNIC</b>	
<b>ELECTRICAL ENGINEERING DEPARTMENT</b>		
<b>ASSIGNMENT</b>		
<b>Course Name (With Code):</b> Fundamentals Of Electronics (4330904)		
<b>Semester / Year:</b> Third / Second		
<b>Assignment Number:</b> 5		
<b>Assignment CO Number:</b> 4330904.5		
<b>Sr. No.</b>	<b>Questions related to Course Outcomes</b>	
<b>Part – A</b>	<b>Questions carrying 3 Marks</b>	
1	Draw and explain block diagram of regulated power supply.	
2	Explain Feedback type series voltage regulator.	
3	Explain shunt type voltage regulator.	
4	What is need for IC's?	
5	State advantages SMPS.	
<b>Part – B</b>	<b>Questions carrying 4 Marks</b>	
1	Explain the Basic circuit of SMPS and write the advantages of SMPS.	
2	State advantages & disadvantages of IC's.	
3	Explain parameters of the regulator and the need of regulated DC power supply.	
4	Explain regulated power supply using IC-7805 & IC-7905.	
5	Explain variable power supply using IC-LM 317.	
<b>Part – C</b>	<b>Questions carrying 7 Marks</b>	
1	Explain Uninterrupted power supply.	
2	Explain three terminal voltage regulators IC.	
3	Draw the functional block diagram of IC 555 and its pin connection .Explain IC 555 as a mono stable multivibrator.	
4	Explain the Basic circuit of SMPS and draw the Block diagram of SMPS	
5	Draw diagram and explain feedback type series voltage regulator.	
Mr. Mahendra G. Vasava		
<b>Prepared By: (Name of Faculty (ies)) with signature</b>		<b>Signature of Head of Department</b>