




This document is a part of Main Course File		Document No.: CFM – 8	
	SARDAR VALLABHBHAI PATEL EDUCATION SOCIETY MANAGED		
	N. G. PATEL POLYTECHNIC		
ELECTRICAL ENGINEERING DEPARTMENT			
ASSIGNMENTS			
Course Name (With Code): Power Electronics and Drives (4350902)			
Semester / Year: Fifth/Third			
Assignment Number: 1			
Assignment CO Number: 4350902.1			
Sr. No.	Questions related to Course Outcomes		
Part – A	Questions carrying 3 Marks		
1	Draw the symbol of GTO, IGBT, MCT, UJT, Diac and Triac.		
2	Explain the working of SCR using two transistor analogy.		
3	Draw and explain the thermal equivalent circuit of SCR.		
4	Draw and explain electrical equivalent circuit of IGBT.		
5	Write comparison between natural and forced commutation.		
Part – B	Questions carrying 4 Marks		
1	Draw and explain construction and working of IGBT using characteristics.		
2	Draw and explain construction and working of UJT using characteristics.		
3	Explain the construction & working of GTO.		
4	Explain turn off characteristics of SCR.		
5	Write short note on MCT.		
Part – C	Questions carrying 7 Marks		
1	State different method of mounting of SCR. Explain any two.		
2	Explain different types of protection of SCR.		
3	What is commutation of SCR? Explain different types of commutation method.		
4	What is thermal resistance? Draw the thermal equivalent circuit of SCR.		
5	Explain the construction and working of GTO. Also, state its applications.		
Rakesh H. Maisuriya			
Prepared By: (Name of Faculty (ies)) with signature		Signature of Head of Department	

This document is a part of Main Course File		Document No.: CFM – 8
	SARDAR VALLABHBHAI PATEL EDUCATION SOCIETY MANAGED N. G. PATEL POLYTECHNIC	
	ELECTRICAL ENGINEERING DEPARTMENT	
ASSIGNMENTS		
Course Name (With Code): Power Electronics and Drives (4350902)		
Semester / Year: Fifth/Third		
Assignment Number: 2		
Assignment CO Number: 4350902.2		
Sr. No.	Questions related to Course Outcomes	
Part – A	Questions carrying 3 Marks	
1	Explain effect of transformer reactance on rectifier circuit.	
2	Write advantages of polyphase rectifier over single phase rectifier.	
3	Write short note on Pulse transformer.	
4	Explain AC load control using two SCRs and two Diodes.	
5	Explain role of electronic regulators and controlled rectifiers in energy conservation.	
Part – B	Questions carrying 4 Marks	
1	Explain three phase half wave rectifier with necessary waveforms.	
2	Derive the equation for Irms and Erms for three phase half wave rectifier.	
3	Explain three phase full wave rectifier with necessary waveforms.	
4	Explain six phase half wave rectifier with necessary waveforms.	
5	What is the need of controlled rectifier? Write the applications of controlled rectifier.	
Part – C	Questions carrying 7 Marks	
1	Enlist the method of firing angle control of SCR. Explain RC phase shift control method.	
2	Explain full wave controlled rectifier using LR phase shift control and RC phase shift control method.	
3	Explain pulse control of SCR using UJT full wave rectifier.	
Rakesh H. Maisuriya		
Prepared By: (Name of Faculty (ies)) with signature		Signature of Head of Department

This document is a part of Main Course File		Document No.: CFM – 8
	SARDAR VALLABHBHAI PATEL EDUCATION SOCIETY MANAGED	
	N. G. PATEL POLYTECHNIC	
ELECTRICAL ENGINEERING DEPARTMENT		
ASSIGNMENTS		
Course Name (With Code): Power Electronics and Drives (4350902)		
Semester / Year: Fifth/Third		
Assignment Number: 3		
Assignment CO Number: 4350902.3		
Sr. No.	Questions related to Course Outcomes	
Part – A	Questions carrying 3 Marks	
1	Explain working principle of chopper.	
2	Draw and explain different configuration of chopper.	
3	Explain class C chopper.	
4	Give classification of inverter.	
5	Compare voltage source inverter and current source inverter.	
Part – B	Questions carrying 4 Marks	
1	Explain class B chopper with circuit diagram and waveform.	
2	Explain single phase series inverter.	
3	Explain single phase full bridge inverter.	
4	Draw and explain 3-level capacitor clamped multilevel inverter with its advantages and disadvantages.	
5	Draw and explain block diagram of solar system using inverter and buck boost converter.	
Part – C	Questions carrying 7 Marks	
1	Draw and explain Jones Chopper and Morgan’s chopper.	
2	Explain different control technique of chopper.	
3	State different methods of PWM control& explain it. Write the advantages of PWM control.	
<p style="text-align: center;">Rakesh H. Maisuriya</p>		
Prepared By: (Name of Faculty (ies)) with signature		Signature of Head of Department

This document is a part of Main Course File		Document No.: CFM – 8
	SARDAR VALLABHBHAI PATEL EDUCATION SOCIETY MANAGED	
	N. G. PATEL POLYTECHNIC	
ELECTRICAL ENGINEERING DEPARTMENT		
ASSIGNMENTS		
Course Name (With Code): Power Electronics and Drives (4350902)		
Semester / Year: Fifth/Third		
Assignment Number: 4		
Assignment CO Number: 4350902.4		
Sr. No.	Questions related to Course Outcomes	
Part – A	Questions carrying 3 Marks	
1	Draw and explain block diagram of electric drive.	
2	Write advantages and disadvantages of electric drive.	
3	Explain single phase dc drive.	
4	Explain single phase half wave converter drive.	
5	Explain regenerative braking in electric drive with its advantages.	
Part – B	Questions carrying 4 Marks	
1	Explain factors to be considered while selecting electric motors for different electric drive.	
2	Explain AC drive with block diagram and write its advantages and disadvantages of electric drive.	
3	Explain variable frequency drive.	
4	Explain speed control of three phase induction motor using chopper.	
5	Explain single phase semi converter drive.	
Part – C	Questions carrying 7 Marks	
1	Explain single phase full converter drive.	
2	Write types of cycloconverter and explain center tapped transformer cyclo converter.	
3	Explain single phase to single phase bridge type cyclo converter with purely resistive load.	
<p style="text-align: center;">Rakesh H. Maisuriya</p>		
Prepared By: (Name of Faculty (ies)) with signature		Signature of Head of Department